

Dr. D. Y. Patil Unitech Society  
Dr. D. Y. Patil Science & Computer Science College,  
Akurdi, Pune - 411 044

DEPARTMENT OF ELECTRONICS

Name : patil sureaj shantaram		REMARKS
Class : sybcs	Roll No. :      Batch :	
Experiment No. :	Performed Date :      /      /20	
Title of Experiment : study of time division multiplexing.		


• Aim :- to study the time division multiplexing.

• Apparatus :- CRO, circuit board, connecting wires, stop watch.


• Formula :-  $\frac{1.44}{(RA + 2RB) * C}$  = calculated frequency

observed frequency =  $C = 10pF$   $\frac{1}{\lambda * t}$

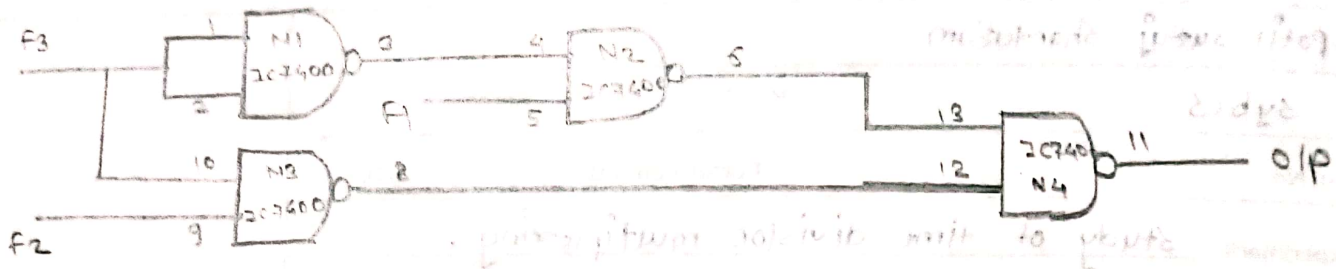circuit diagram time division multiplexing :-



circuit for generating frequency :-

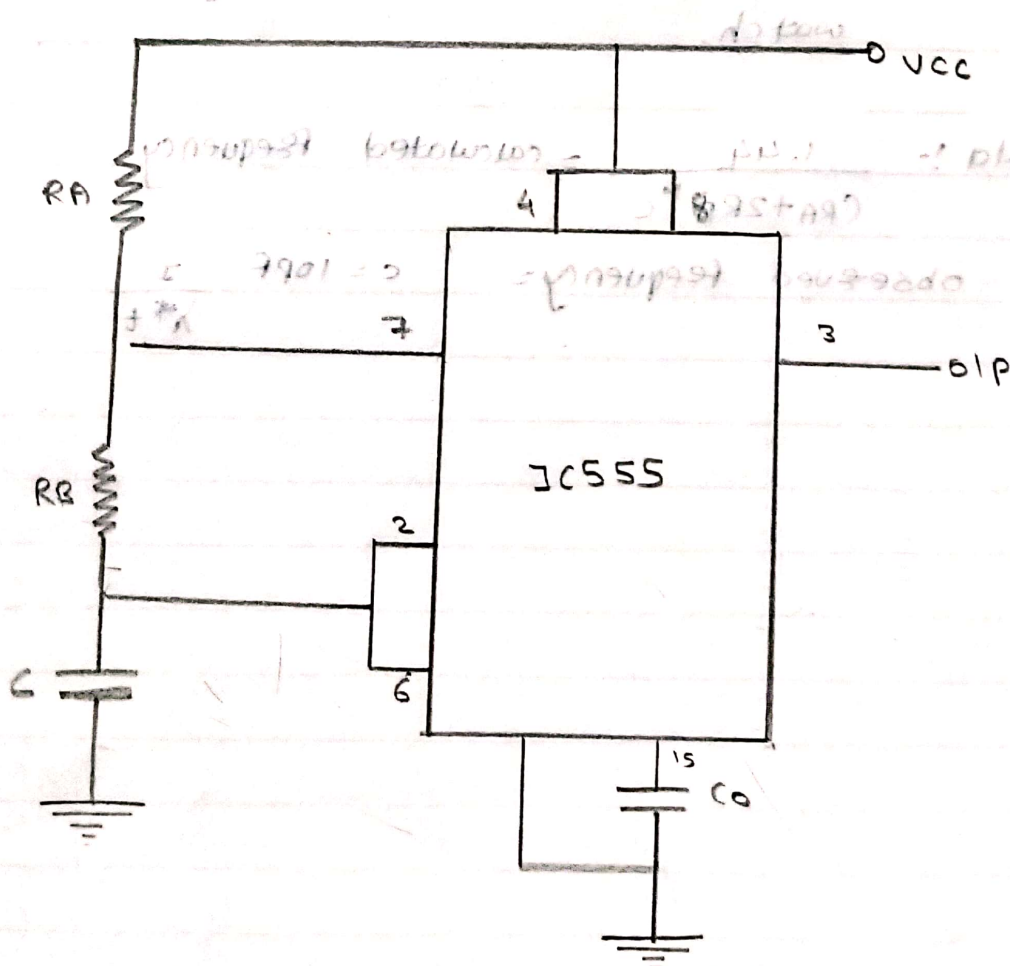



### • procedure :-

- 1] connect the circuit as shown in fig.
- 2] Before switching ON calculate  $f_1, f_2, f_3$  by using formula.
- 3] now connect CRO between pin 3 ground and measure frequency  $f_1$ .
- 4] connect CRO between 11 of 7400 and GND observe that frequency  $f_1$  and  $f_2$  alternatively after particular interval and calculate frequency  $f_3$  from that time measure frequency  $f_3$  by using stopwatch.
- 5] theoretical and practical value of  $f_1, f_2, f_3$  and write suitable conclusion.

### • Truth table :-

control frequency $f_3$	i/p frequency	o/p frequency.
High level 1	$f_1$ and $f_2$	$f_2$
low level 0	$f_1$ and $f_2$	$f_1$

### • theory :-


The time division multiplexing means selection of different frequency after particular interval of time. In this circuit there are three frequency  $f_1, f_2, f_3$  is also called control frequency and with the help of  $f_3$  selection of  $f_1$  &  $f_2$  is carried out.

this concept can be explained as follows :-

\* truth table of NAND gate :-

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

\* multiplying circuit :-

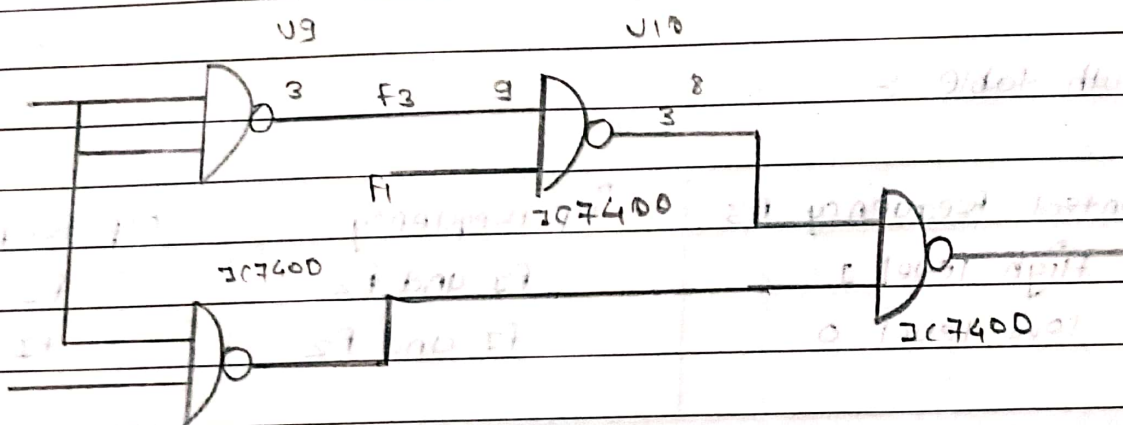

\* observed frequency :-

frequency	$T_{ON}$	$T_{OFF}$	$\lambda = T_{ON} + T_{OFF}$	(t) time/div	$T = \lambda^4$	$F = 1/T$
F1	2.2	2	4.2	0.5 $\mu s$	$2.1 \times 10^{-3}$	0.476 KHz
F2	2.4	2.2	4.6	0.2 $\mu s$	$0.92 \times 10^{-3}$	0.086 KHz
F3	-	-	-	-	4.2	0.00283 KHz



• calculations :- for  $F_1$ ,

$$T_{ON} = 2.2, T_{OFF} = 2, 0.5 \mu s = t$$

$$T = \lambda * t$$

$$= 4.2 \times 0.5 \times 10^{-3}$$

$$= 2.1 \times 10^{-3}$$

$$F_1 = \frac{1}{2.1 \times 10^{-3}} = 0.476 \text{ KHz.}$$

for  $F_2$ ,

$$T_{ON} = 2.4, T_{OFF} = 2.2, 0.2 \mu s = t$$

$$\lambda = 2.4 + 2.2 = 4.6$$

$$T = \lambda * t$$

$$= 4.6 \times 0.2 \times 10^{-3}$$

$$= 0.92 \times 10^{-3}$$

$$F_2 = \frac{1}{0.92 \times 10^{-3}} = 1.086 \text{ KHz.}$$

for  $F_3$ ,

$$T = 4.2$$

$$F_3 = \frac{1}{4.2} = 0.2380 \text{ Hz}$$

$$= 0.00283 \text{ KHz.}$$

★ Result :-

	calculated frequency	observed frequency.
$F_1$	0.476 KHz	0.476 KHz
$F_2$	1.086 KHz	1.086 KHz
$F_3$	0.00283 KHz	0.00283 KHz.

\* conclusion :-

1. we have studied TDM (time division multiplexing).
2. in TDM each signal can occupy entire BW and channel it is allotted a small time slot. Hence multiple signals are transmitted over channel turn by turn. i.e. signal  $f_1, f_2, f_3$ .
3. where  $f_1$  and  $f_2$  are signal frequency and  $f_3$  is control frequency.
4.  $f_1, f_2$  and  $f_3$  is generated by using IC755 in a stable mode.
5. Frequency is decided by value of  $R_A, R_B$  &  $C$   
$$f = \frac{1.44}{(R_A + 2R_B) * C}$$
6. Hence by changing value of  $R_A$  &  $R_B$  &  $C$  frequency can be changed.
7. when  $f_3 = 0$ ,  $f_1$  will pass.  
 $f_1 = 1$ ,  $f_2$  will pass.



Roll No.

Expt. No.

On x axis, 1 cm =  
Scale

On y axis, 1 cm =

Title of the Graph : TDM

3.0